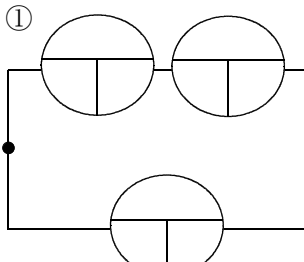
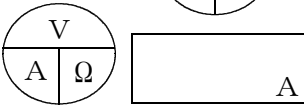



/	解説
/	NO14


中2理科電流と電圧 NO7
 オーム坊や計算用紙②


NAME	

Aコース



①  

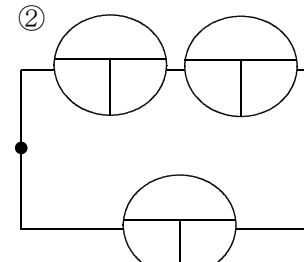
②  A

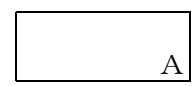
③  A

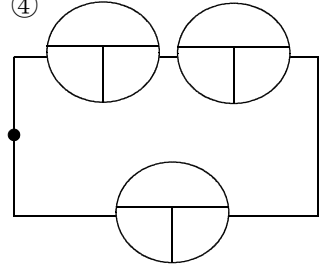
④  A

Bコース

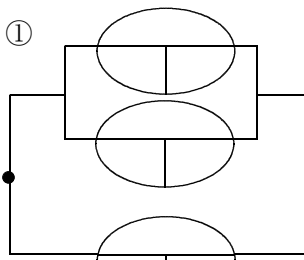
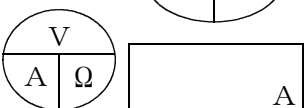
①  

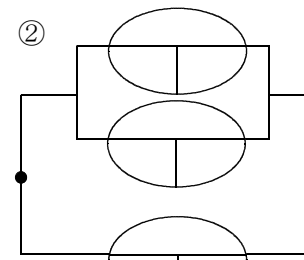
②  A


③  A

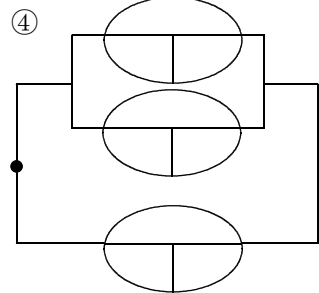
④  A

Cコース

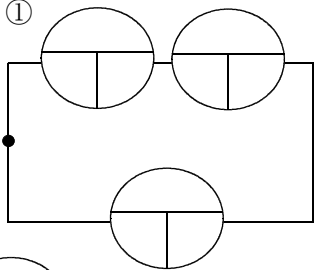
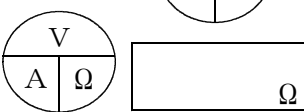
①  

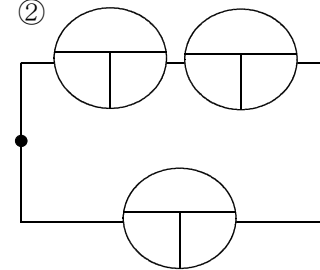
②  Ω

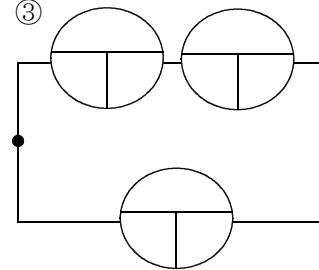
③  Ω

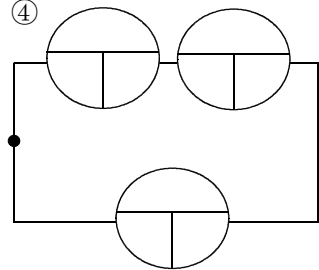
④  Ω

Dコース

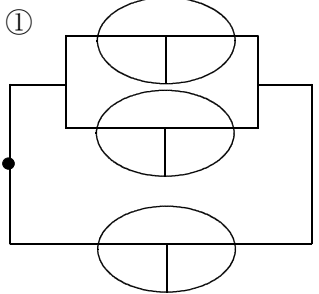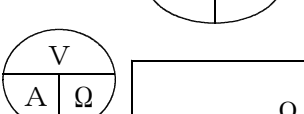①  

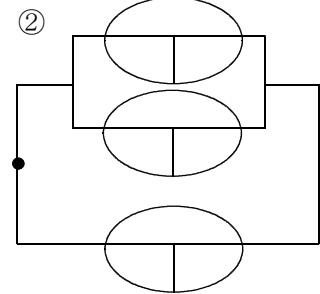②  Ω

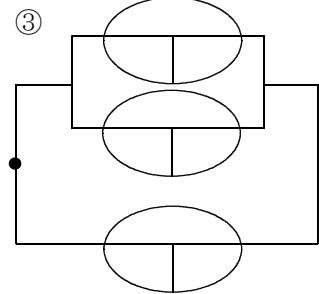③  Ω

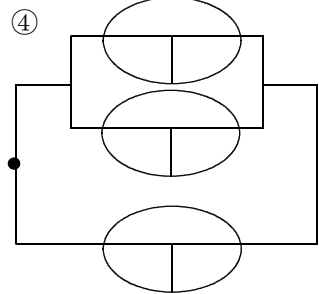④  Ω