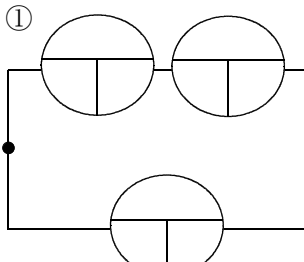
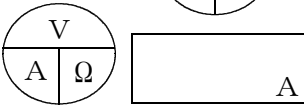


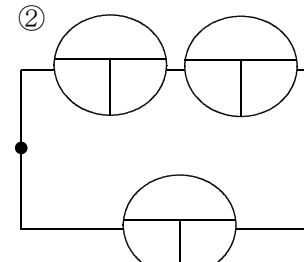
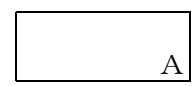
/	解説
/	NO14

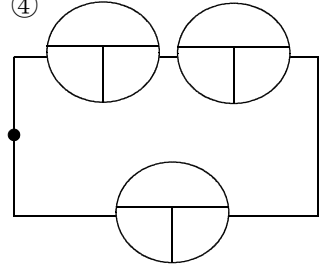
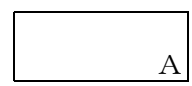
中2理科電流と電圧 NO7  
 オーム坊や計算用紙③

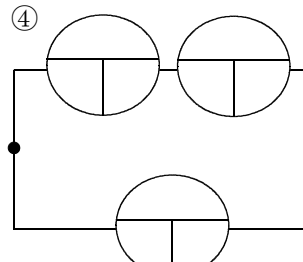
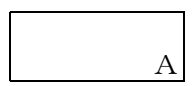
NAME	

**Aコース**

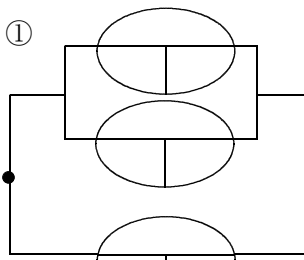
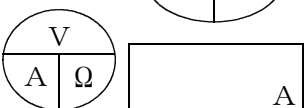
①  

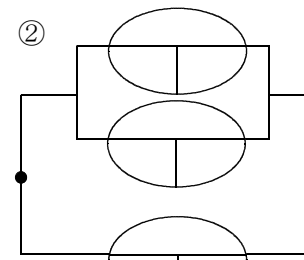

②  

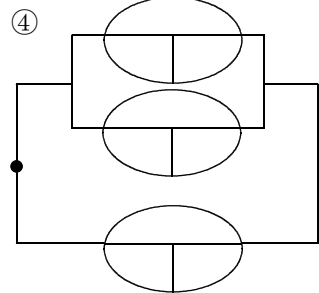

③  

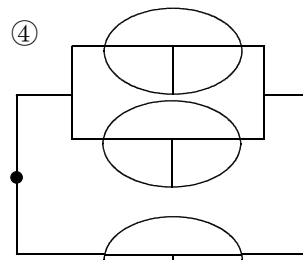

④  

**Bコース**

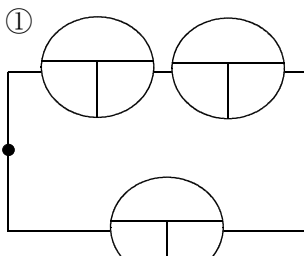
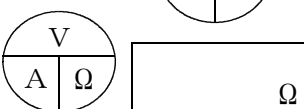
①  

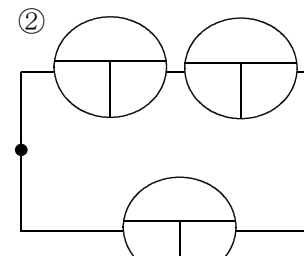

②  

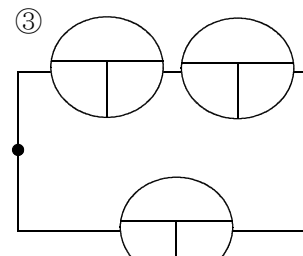

③  

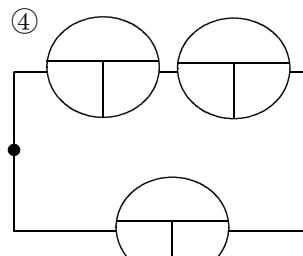

④  

**Cコース**

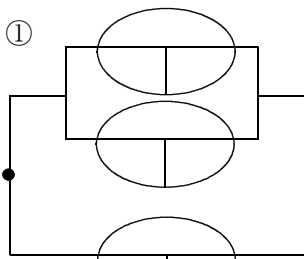

①  

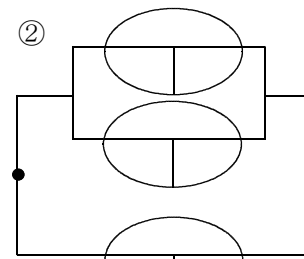

②  

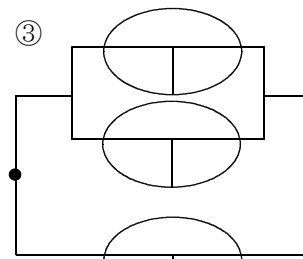

③  

④  

**Dコース**

①  

②  

③  

④ 